
4-bit incrementer**X58456_en**

Design a circuit that receives a 4-bit number and produces the same number increased by one unit ($\text{mod } 16$).

Specification

```
module incr4(in, out);
    input [3:0] in;
    output [3:0] out;
```

Input

- *in* represents the 4-bit input number.

Output

- *out* represents the 4-bit output number.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:59

© Jutge.org, 2006–2013.

<http://www.jutge.org>